

EXPERIMENT-3



AIM: To verify the operation of a half and full adder.

HARDWARE / SOFTWARE APPARATUS : Power supply , bread board , connecting wires , respective IC

(7408,7486)


CIRCUIT:

AND GATE

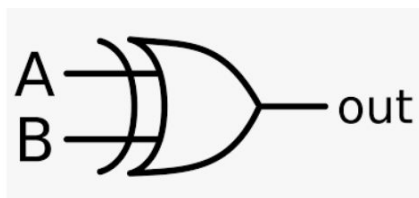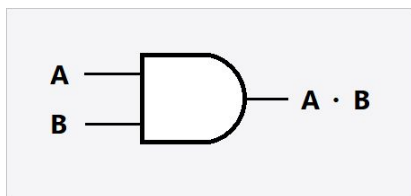


PIN-DIAGRAM:

AND GATE

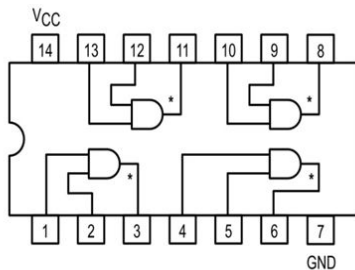

XOR GATE

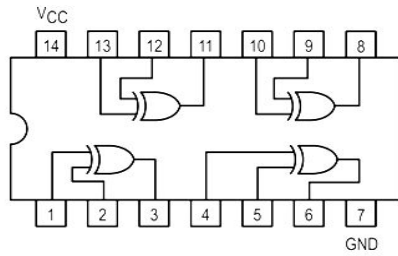

TRUTH TABLE:

AND Truth Table		
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

XOR Truth Table		
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Input			Output	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

THEORY: Half adder can add two bits individually. The output of a half adder has a sum bit and carries for the sum bit.

Similarly, the full adder can be used to add three bits together.

Both these adders can be formed by using the logic gates of and and xor.


The full adder can also be seen as a sum of two individual half adders.

PROCEDURE (MULTISIM):

- Select the required gate symbol from the digital section of the tool bar on the left .
- Select a resistor from the same toolbar.
- Select the voltage sources and ground symbols from that toolbar.
- Ground both the voltage sources(clock) and then connect them to the input terminal of the gate.
- Connect the output terminal to 1kohm resistor and ground it.

CIRCUIT DIAGRAMS:

HALF ADDER

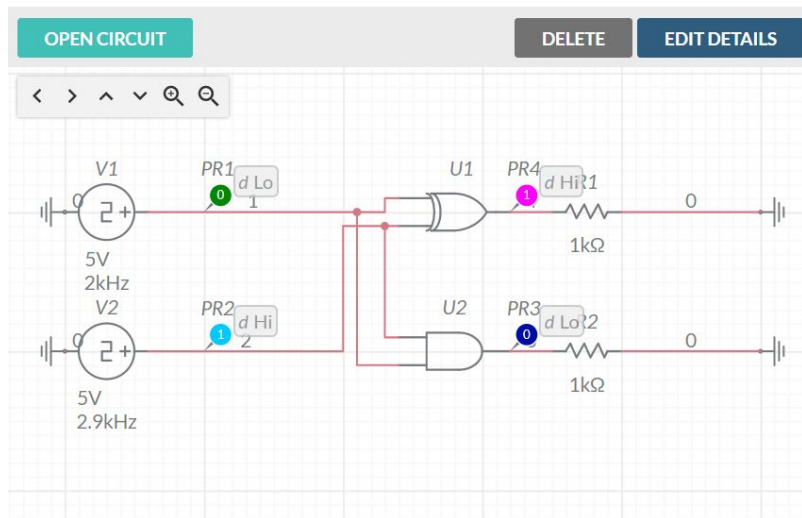

CREATOR



therijulsharma
27 Circuits

DATE CREATED

5 days ago

LAST MODIFIED

5 days ago

FOLDER


STLD experiment 3

TAGS

This circuit has no tags currently.

EDIT TAGS

FULL ADDER

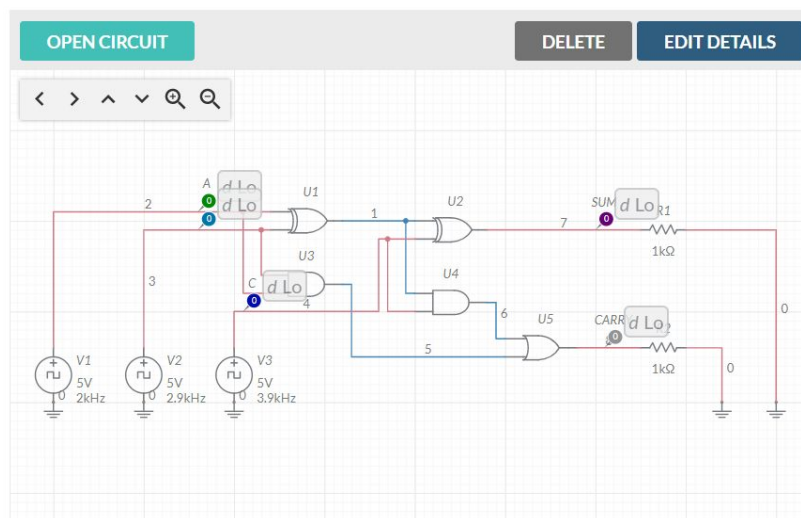

CREATOR



therijulsharma
27 Circuits

DATE CREATED

4 days, 23 hours ago

LAST MODIFIED

4 days, 23 hours ago

FOLDER

STLD experiment 3

TAGS


This circuit has no tags currently.

EDIT TAGS


INPUT /OUTPUT WAVEFORMS:

HALF ADDER

Circuit Graph

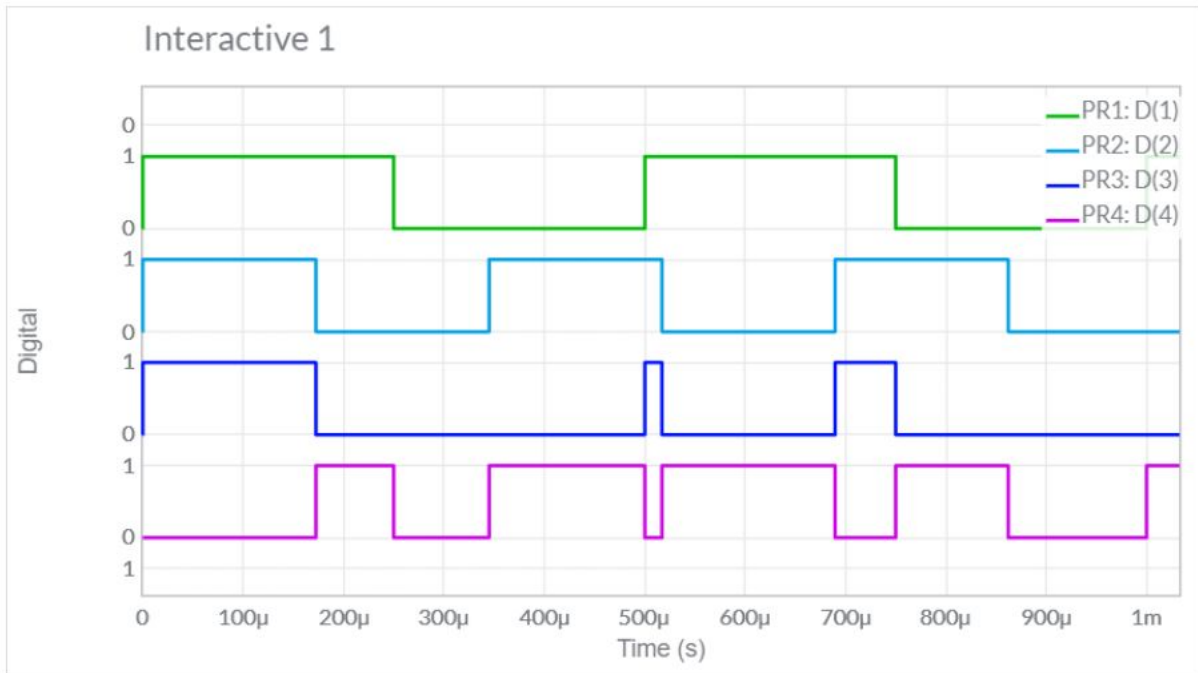

FULL ADDER

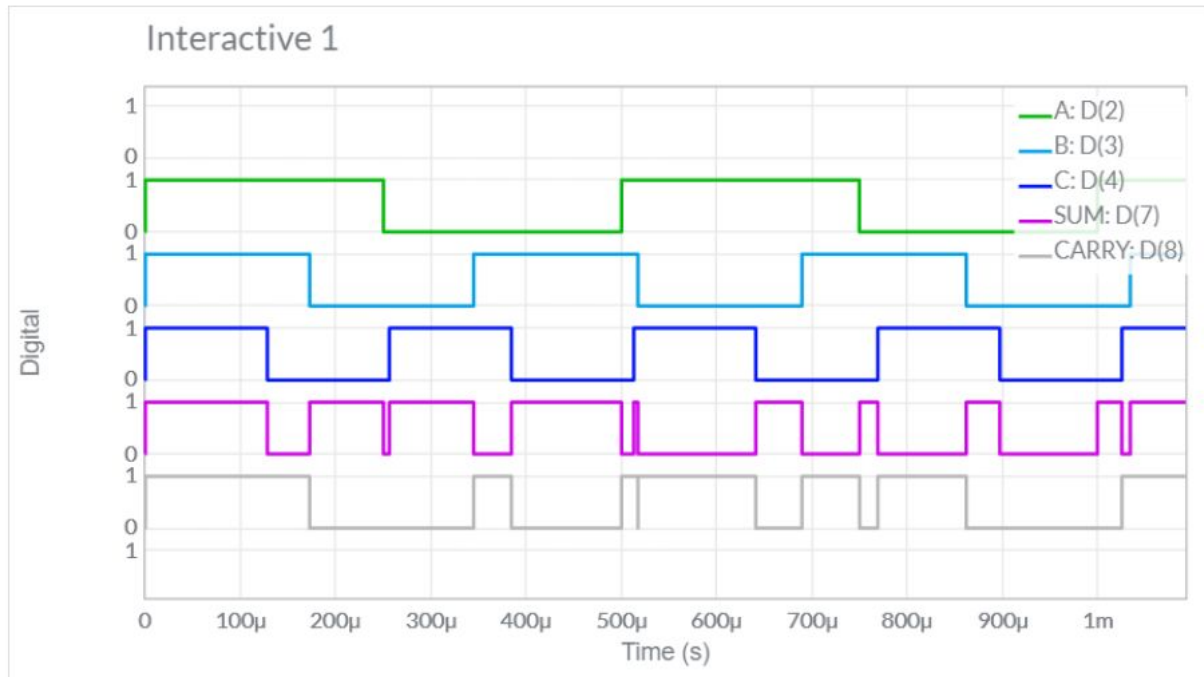**PRECAUTIONS:**

- Power supply should not exceed than 5V.
- Connections should be tight.
- Components should be tested before the practical.