

# EXPERIMENT-1


**AIM:** To verify the truth tables of all logical gates (AND ,OR ,NOT ,NAND , NOR , XOR, XNOR).

**HARDWARE / SOFTWARE APPARATUS :** Power supply , Bread Board , Connecting Wires, respective IC


(7404, 7408, 7432, 7486, 7400, 7402, 74266)

**CIRCUIT:**


AND GATE

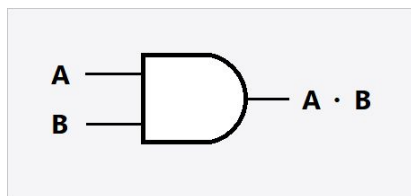


OR GATE

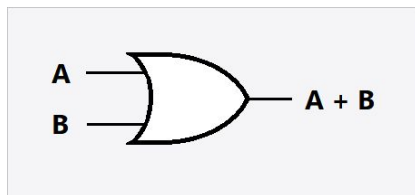


NAND GATE

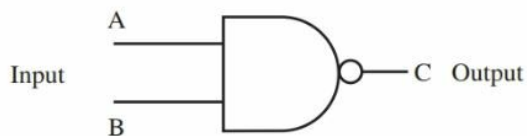


NOR GATE

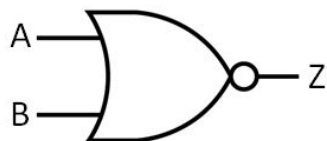


XOR

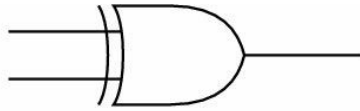

XNOR

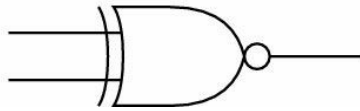


NOT GATE

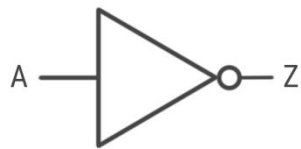


**PIN-DIAGRAM:**


**AND GATE**

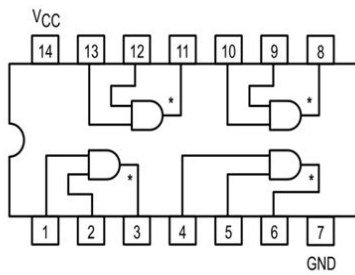


**NAND GATE**

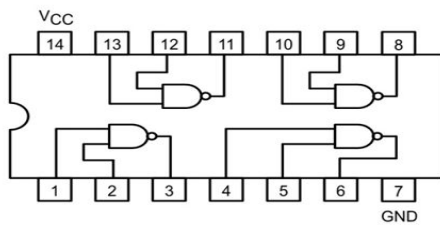


**OR GATE**

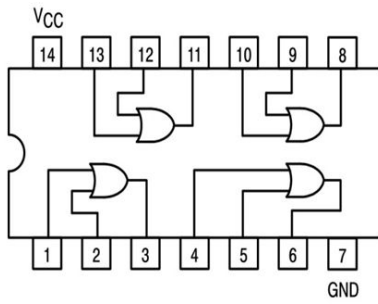


## NOR GATE

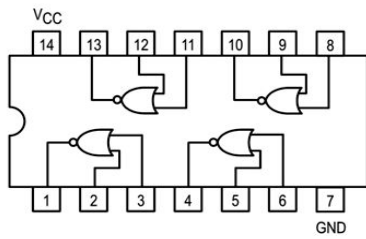


## XOR GATE

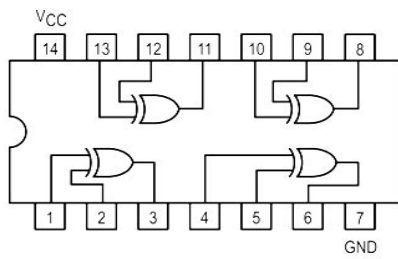

## XNOR GATE

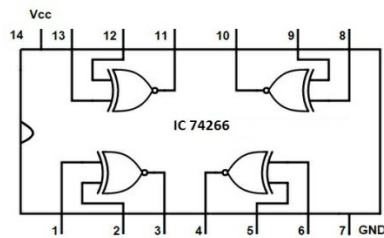

## NOT GATE

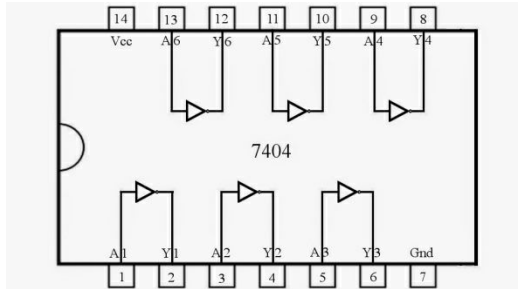

## TRUTH TABLE:

### AND GATE

AND Truth Table		
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

### NAND GATE

NAND Truth Table		
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

### OR GATE

Or Truth Table		
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

## NOR GATE

NOR Truth Table		
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

## XOR GATE

XOR Truth Table		
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

## XNOR GATE

XNOR Truth Table		
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

## NOT GATE

NOT Truth Table	
A	Q
0	1
1	0


**THEORY:** Logic gates are electronic circuits which perform logical operations on one or more inputs to produce a signal output. There are 7 logic gates. These include the AND, NAND, OR, NOR, XOR, XNOR and NOT.

## PROCEDURE (MULTISIM):

- Select the required gate symbol from the digital section of the tool bar on the left .
- Select a resistor from the same toolbar.
- Select the voltage sources and ground symbols from that toolbar.
- Ground both the voltage sources(clock) and then connect them to the input terminal of the gate.
- Connect the output terminal to 1kohm resistor and ground it.

## CIRCUIT DIAGRAMS:

AND GATE

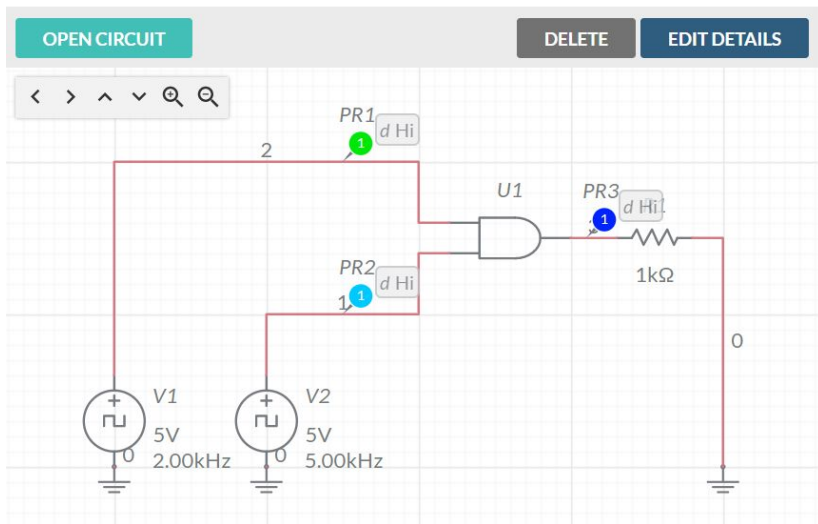

CREATOR

therijulsharma  
7 Circuits


DATE CREATED  
23 minutes ago

LAST MODIFIED  
13 minutes ago

TAGS

This circuit has no tags currently. [EDIT TAGS](#)

NAND GATE

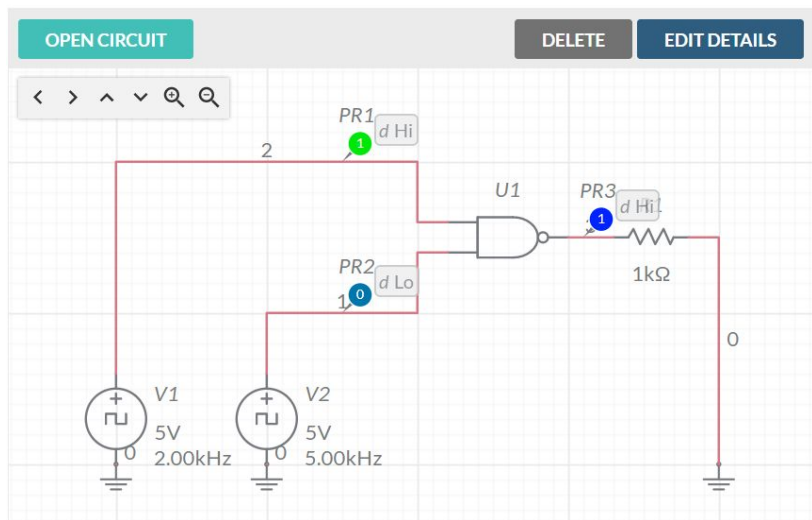

CREATOR

therijulsharma  
7 Circuits

DATE CREATED  
22 minutes ago


LAST MODIFIED  
17 minutes ago

TAGS


This circuit has no tags currently. [EDIT TAGS](#)

CIRCUIT COPIED FROM  
And Gate


OR GATE

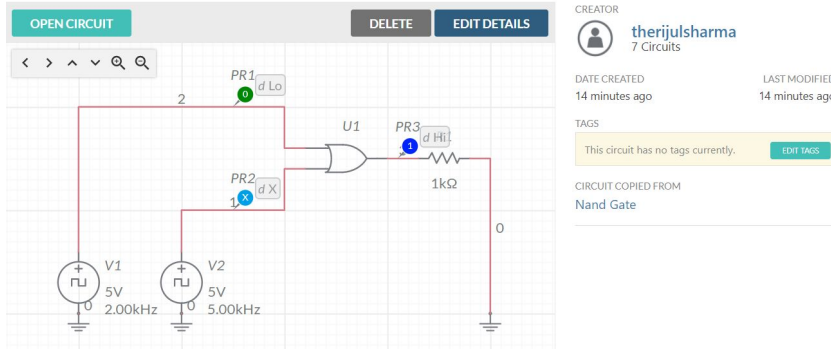

## NOR GATE

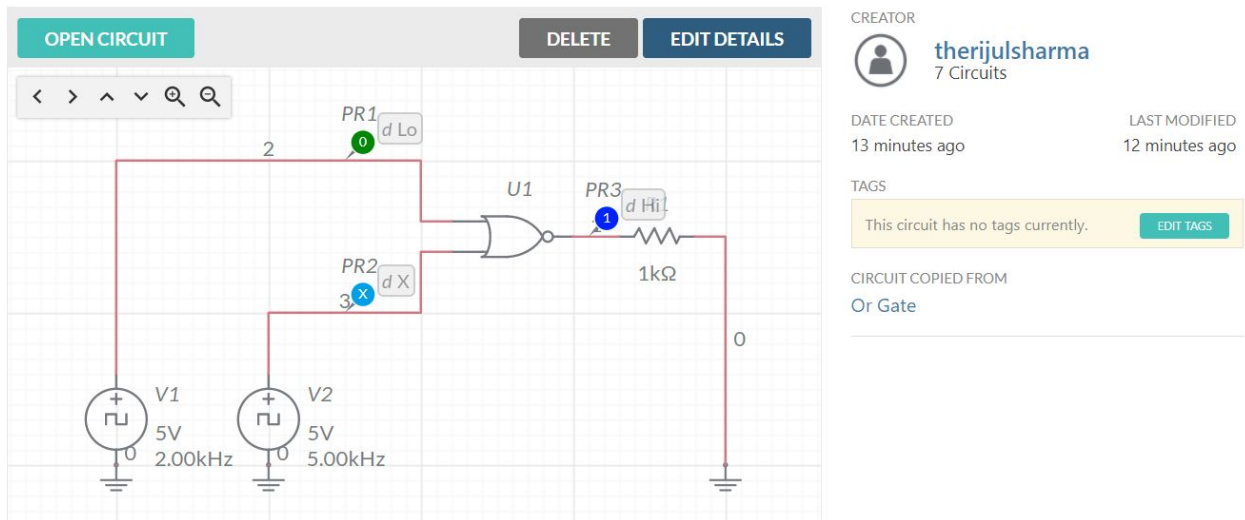


## XOR GATE

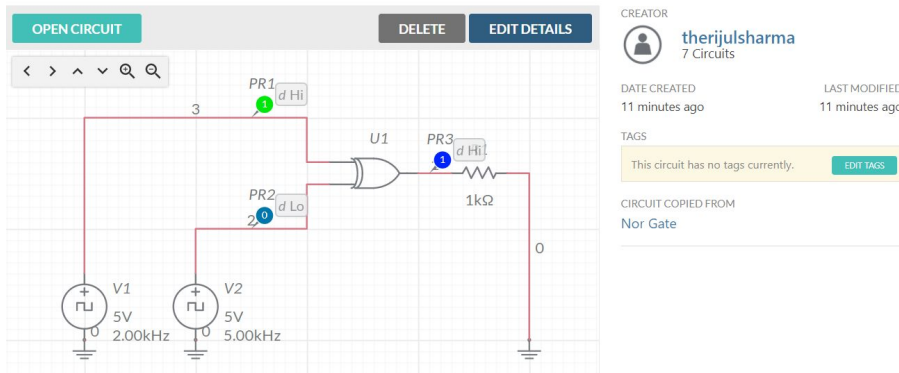

## XNOR GATE



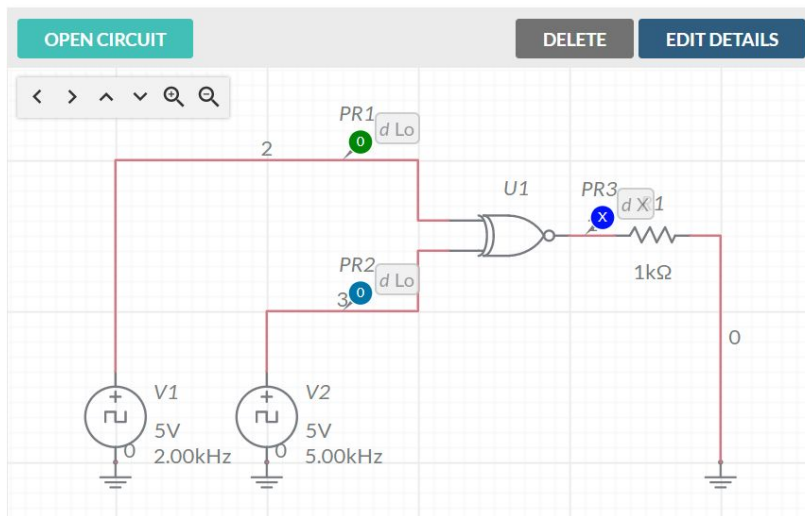

CREATOR



**therijulsharma**  
7 Circuits

DATE CREATED  
11 minutes ago

LAST MODIFIED  
11 minutes ago


TAGS

This circuit has no tags currently.

[EDIT TAGS](#)

CIRCUIT COPIED FROM  
Xor Gate

## NOT GATE

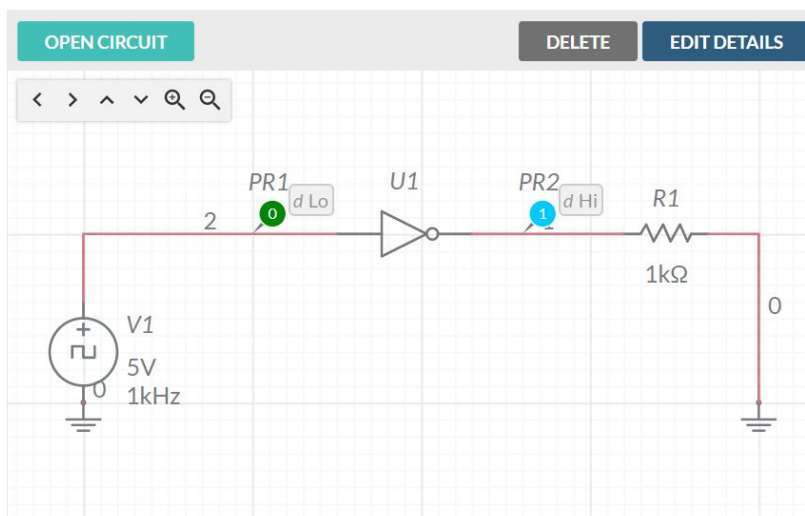

CREATOR



**therijulsharma**  
7 Circuits

DATE CREATED  
8 minutes ago

LAST MODIFIED  
8 minutes ago

TAGS


This circuit has no tags currently.

[EDIT TAGS](#)


## INPUT /OUTPUT WAVEFORMS:

## AND GATE

## Circuit Graph

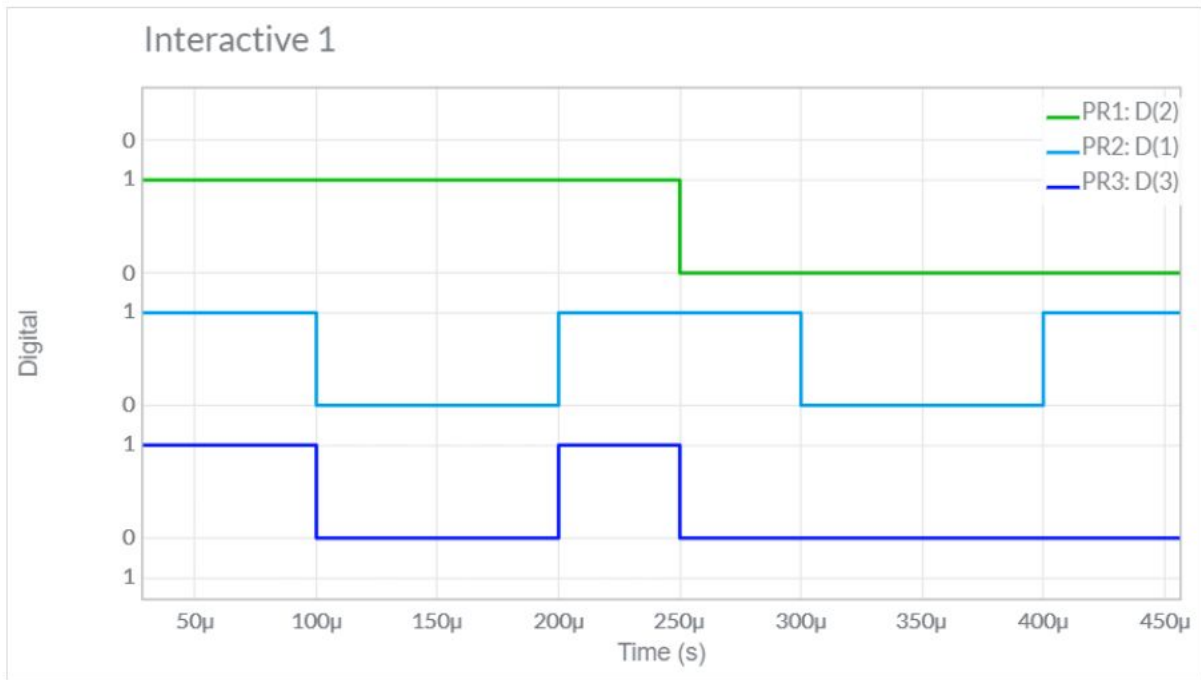

## NAND GATE

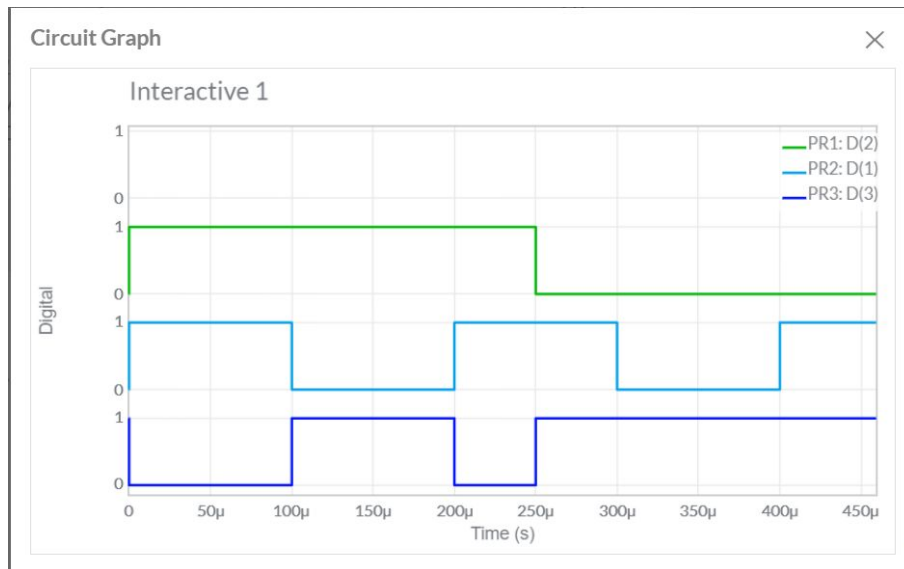


## OR GATE

## Circuit Graph



### Interactive 1

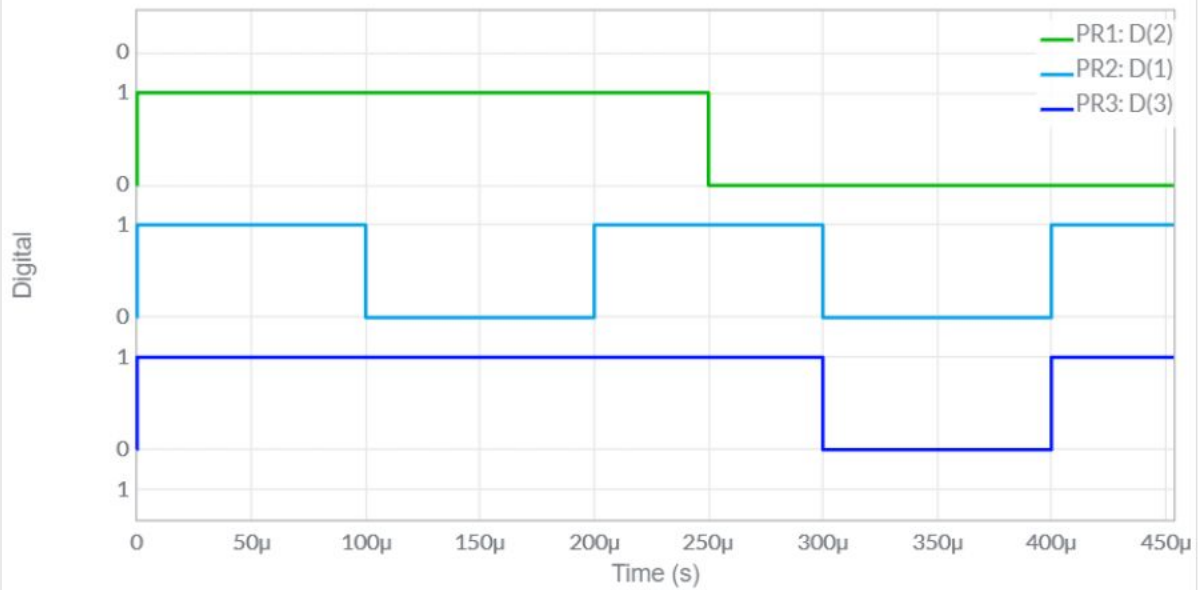


## NOR GATE

### Circuit Graph



### Interactive 1

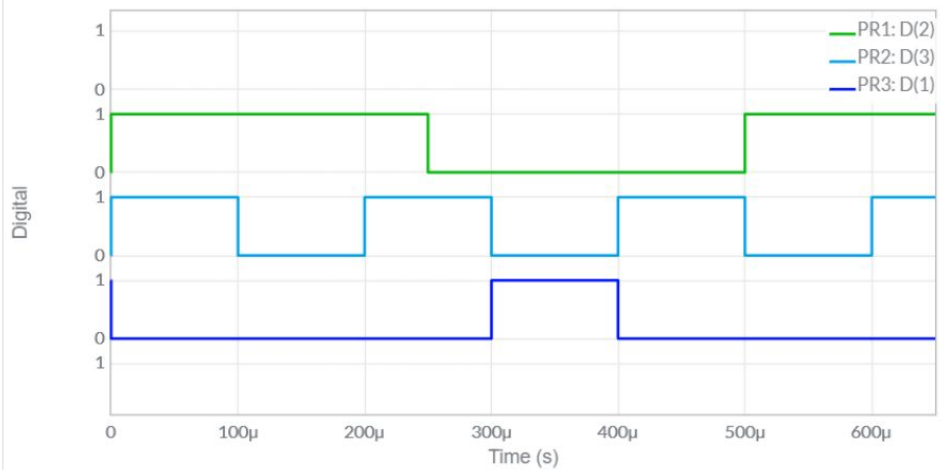


## XOR GATE

## Circuit Graph



### Interactive 1

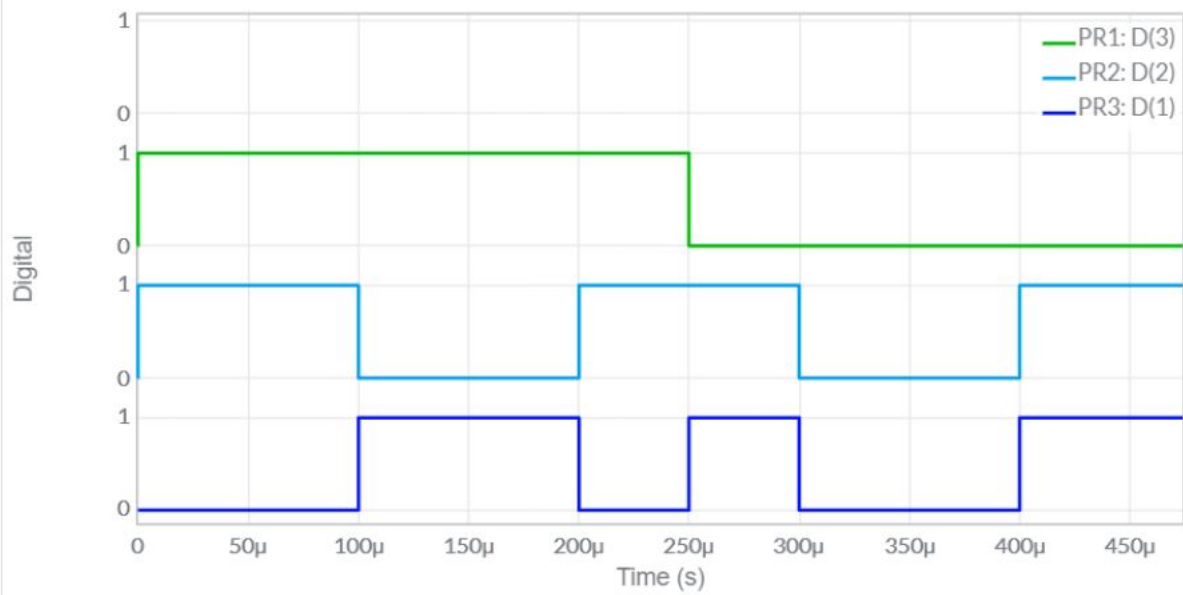


## XNOR GATE

### Circuit Graph




#### Interactive 1

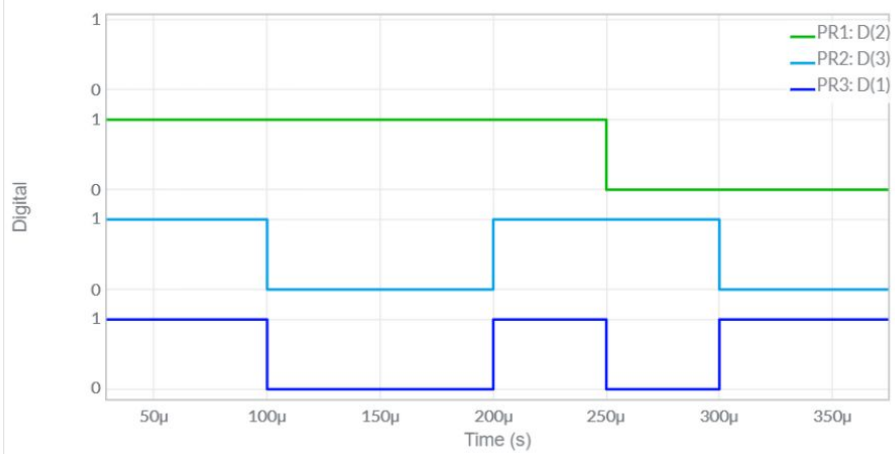

## NOT GATE

## Circuit Graph

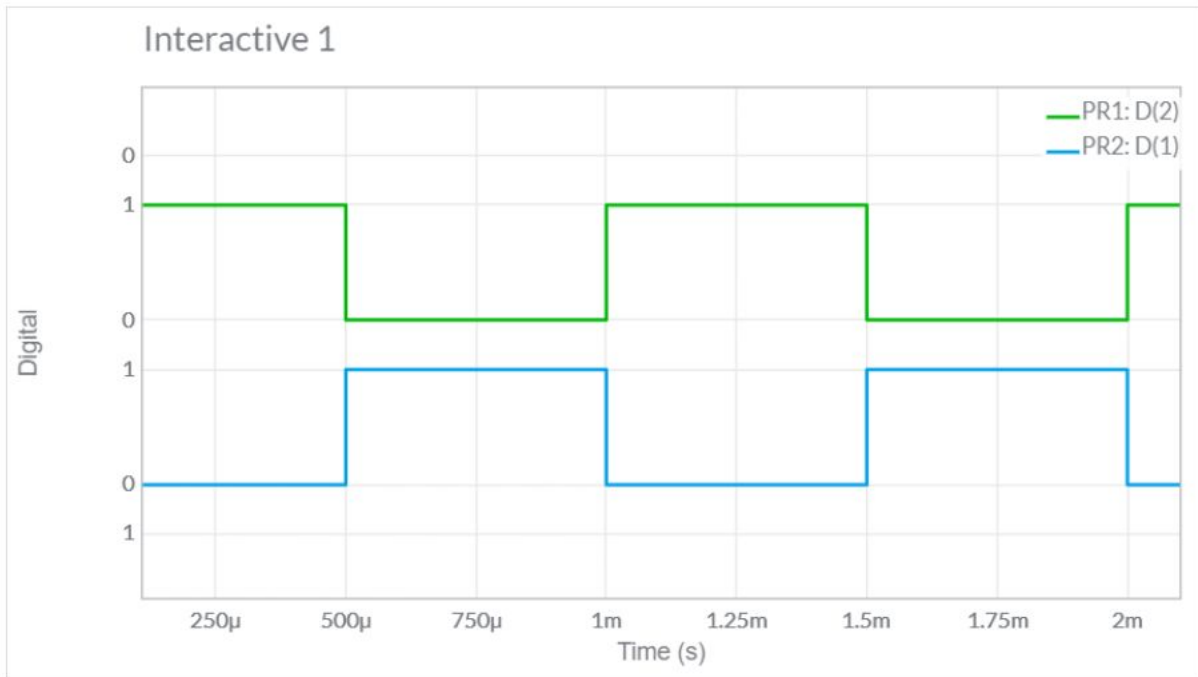

## PRECAUTIONS:

- Power supply should not exceed 5V.
- All the connections should be tight.
- Components should be tested before the practical.