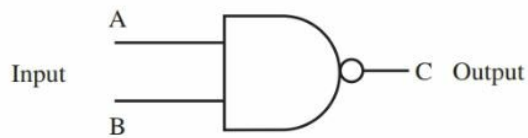


# EXPERIMENT-2a


**AIM:** To realize all the gates using NAND gate

**HARDWARE / SOFTWARE APPARATUS :** Power supply , Bread Board , Connecting Wires, respective IC (7400)

**CIRCUIT:**



**PIN-DIAGRAM:**

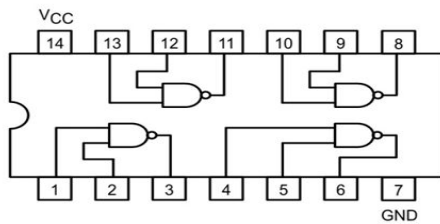

**TRUTH TABLE:**

NAND Truth Table		
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

**THEORY:** NAND gate is actually a combination of two logic gates: AND and NOT gate its output is complement of AND gate


This gate can have a minimum of two inputs while the output is limited to one. Using this gate, we can realise all other gates. This is why this gate is also known as a universal gate.

## PROCEDURE (MULTISIM):

- Select the gate symbol from the digital section of the tool bar on the left .
- Select a resistor from the same toolbar.
- Select the voltage sources and ground symbols from that toolbar.
- Ground both the voltage sources(clock) and then connect them as in the circuit diagram so as to recreate a different gate.
- Connect the output terminal to 1kohm resistor and ground it.

## CIRCUIT DIAGRAMS:

### AND GATE

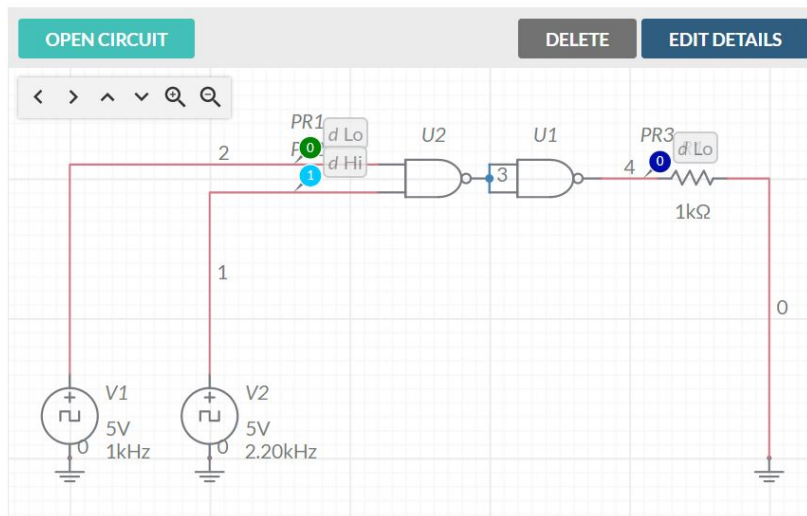

CREATOR



therijulsharma  
13 Circuits

DATE CREATED  
36 minutes ago

LAST MODIFIED  
36 minutes ago


FOLDER  
STLD experiment 2a

TAGS

This circuit has no tags currently.

EDIT TAGS

### OR GATE

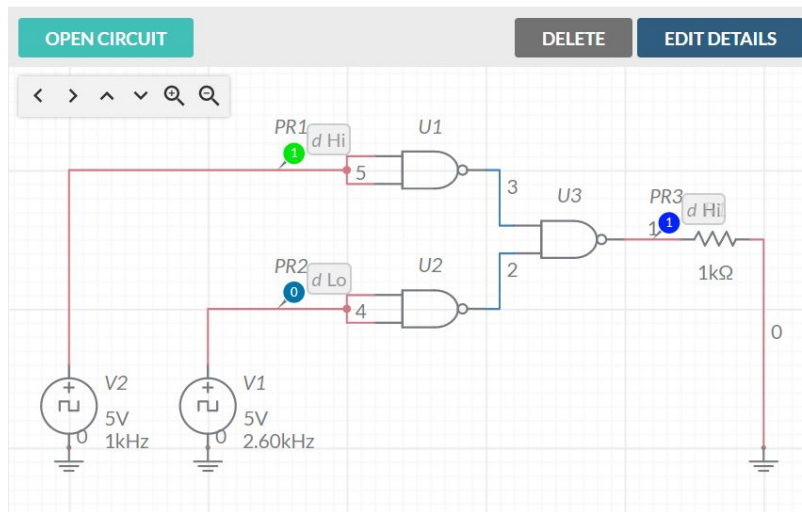

CREATOR



**therijulsharma**  
13 Circuits

DATE CREATED

28 minutes ago

LAST MODIFIED

28 minutes ago

FOLDER


STLD experiment 2a

TAGS

This circuit has no tags currently.

EDIT TAGS

## NOR GATE

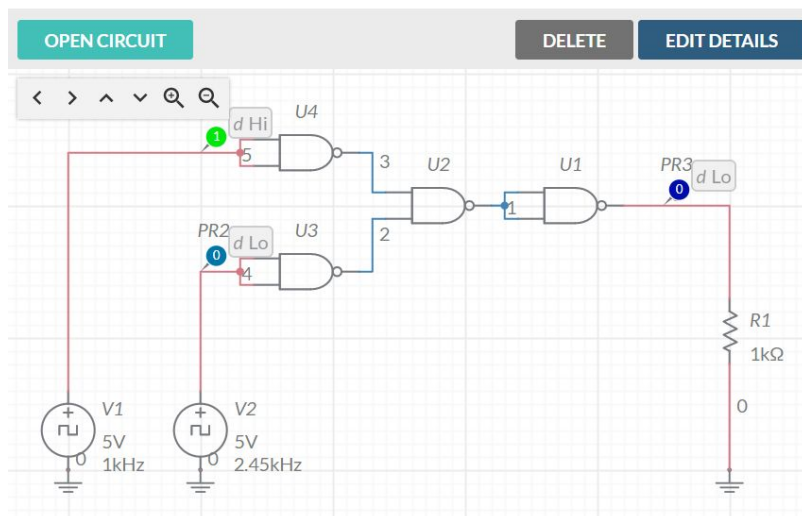

CREATOR



**therijulsharma**  
13 Circuits

DATE CREATED

2 minutes ago

LAST MODIFIED

2 minutes ago

FOLDER


STLD experiment 2a

TAGS

This circuit has no tags currently.

EDIT TAGS

## XOR GATE

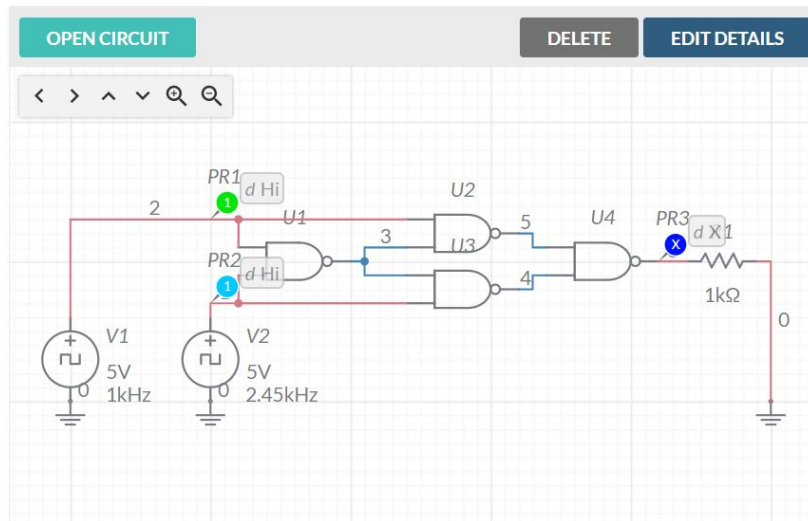

CREATOR



**therijulsharma**  
13 Circuits

DATE CREATED

22 minutes ago

LAST MODIFIED

22 minutes ago

FOLDER


STLD experiment 2a

TAGS

This circuit has no tags currently.

[EDIT TAGS](#)

## XNOR GATE

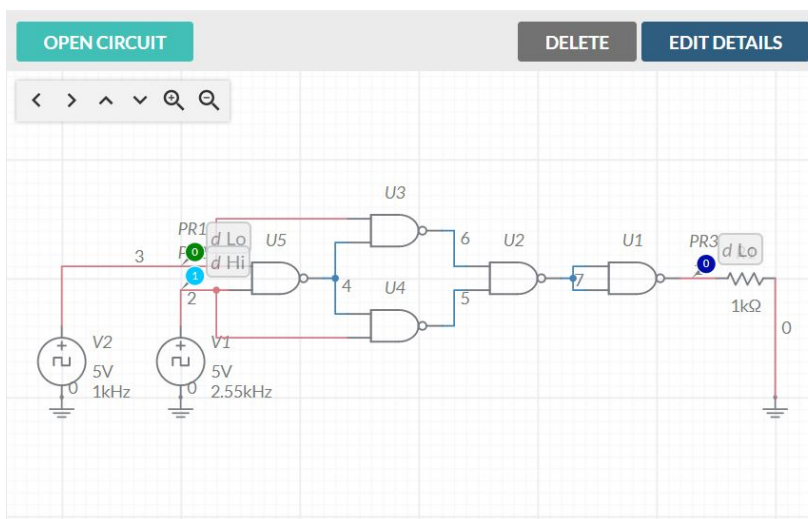

CREATOR



**therijulsharma**  
13 Circuits

DATE CREATED

15 minutes ago

LAST MODIFIED

15 minutes ago

FOLDER


STLD experiment 2a

TAGS

This circuit has no tags currently.

[EDIT TAGS](#)


## NOT GATE

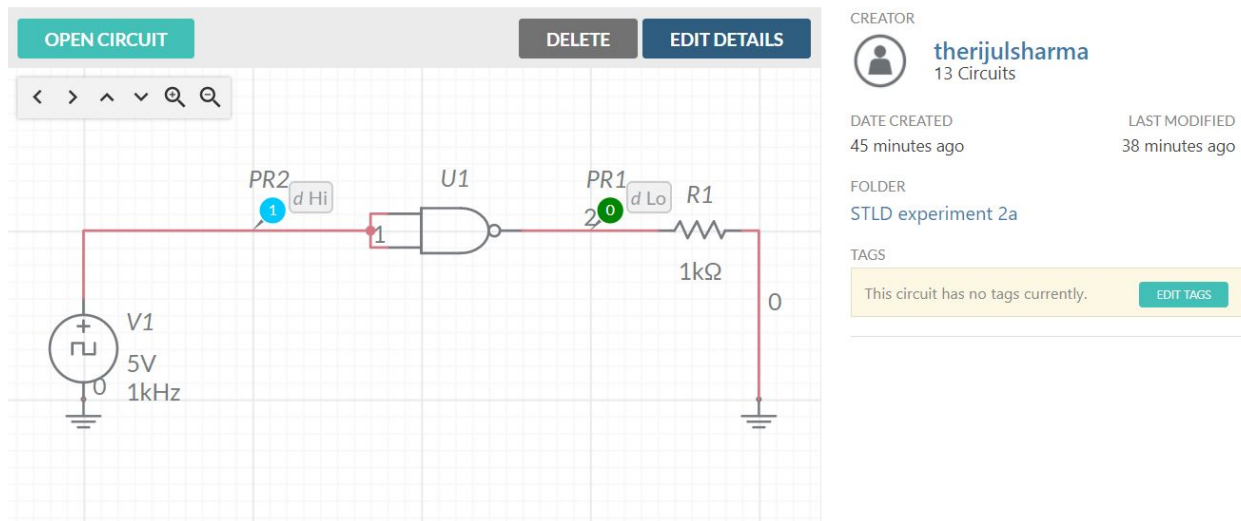


## INPUT /OUTPUT WAVEFORMS:

### AND GATE


Circuit Graph

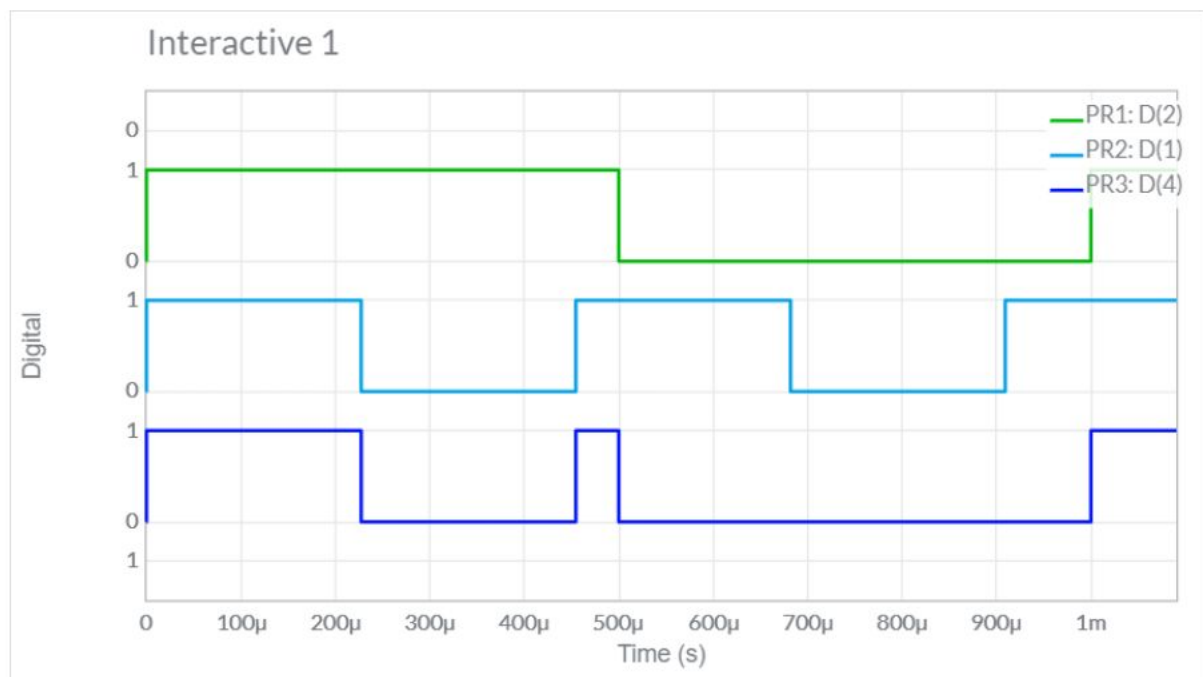

### OR GATE

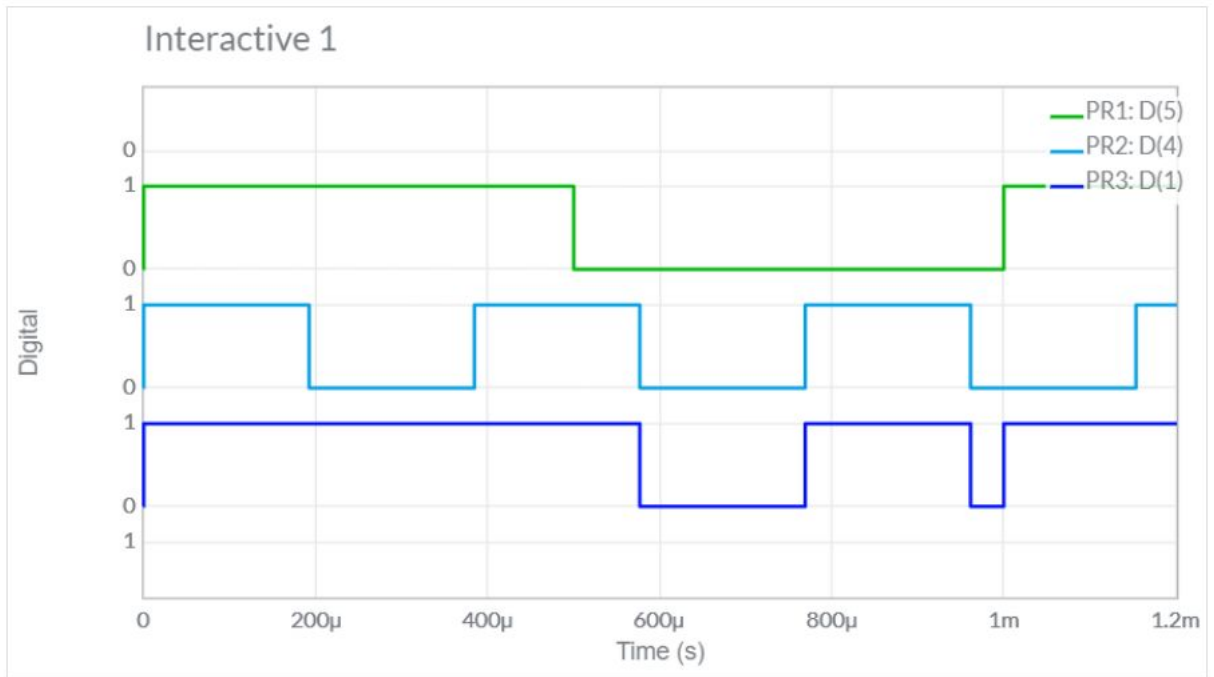


**NOR GATE**

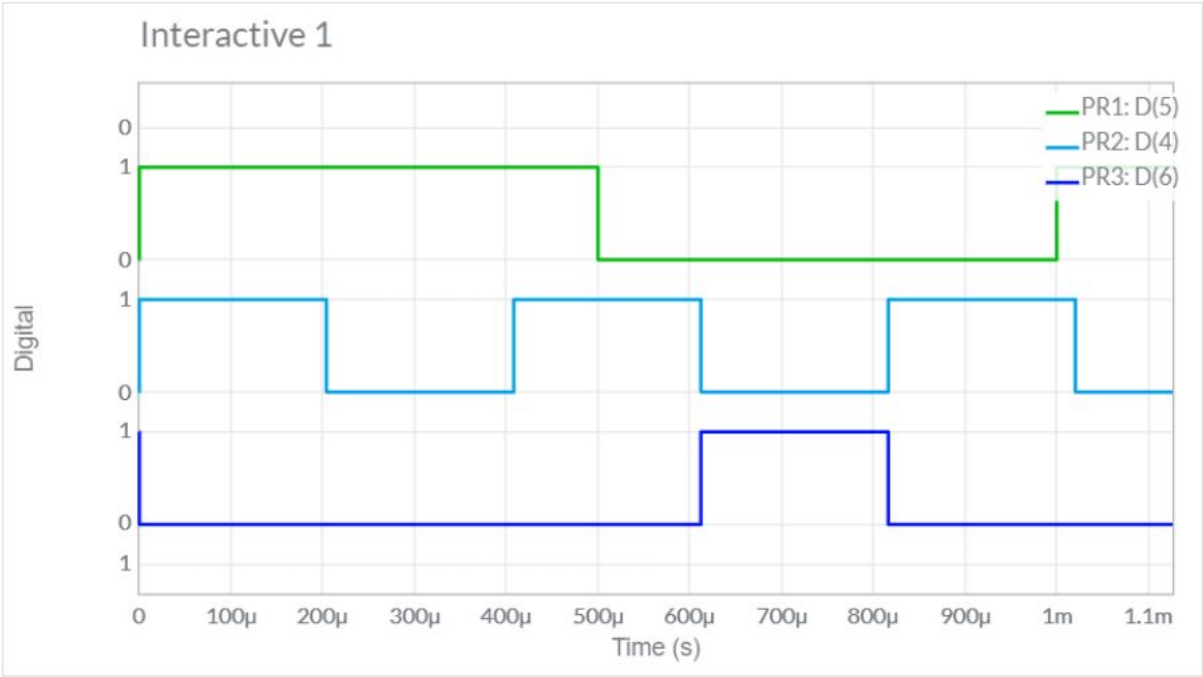

XOR GATE


## Circuit Graph

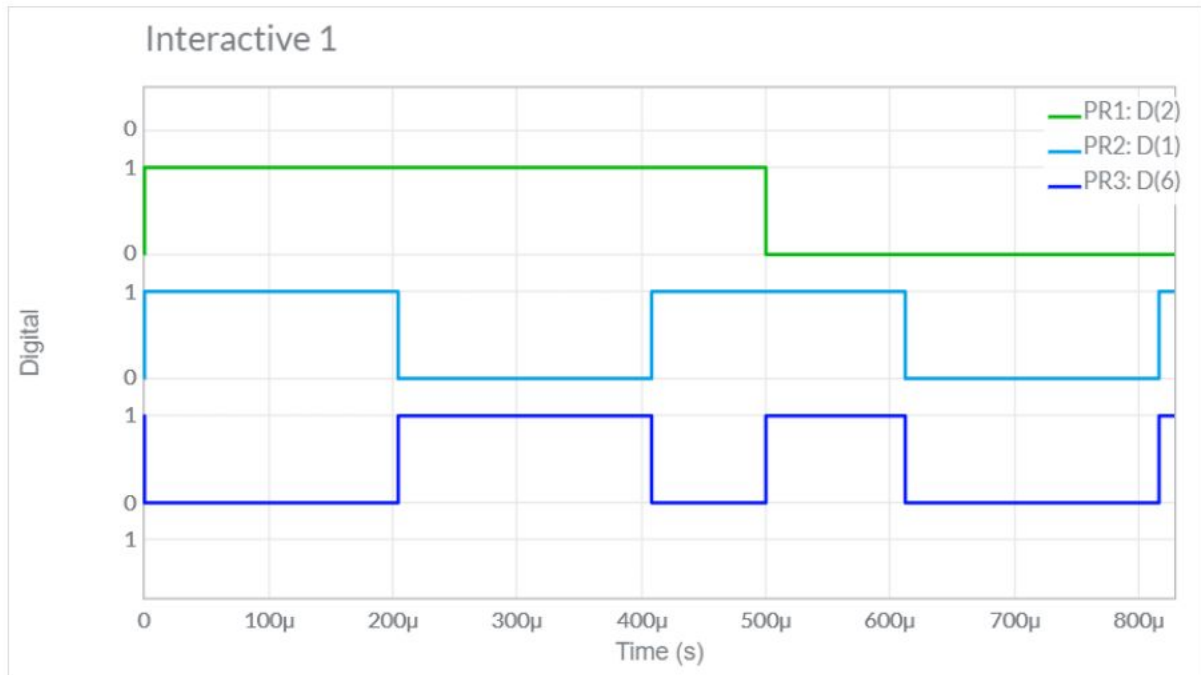

## XNOR GATE




## Circuit Graph

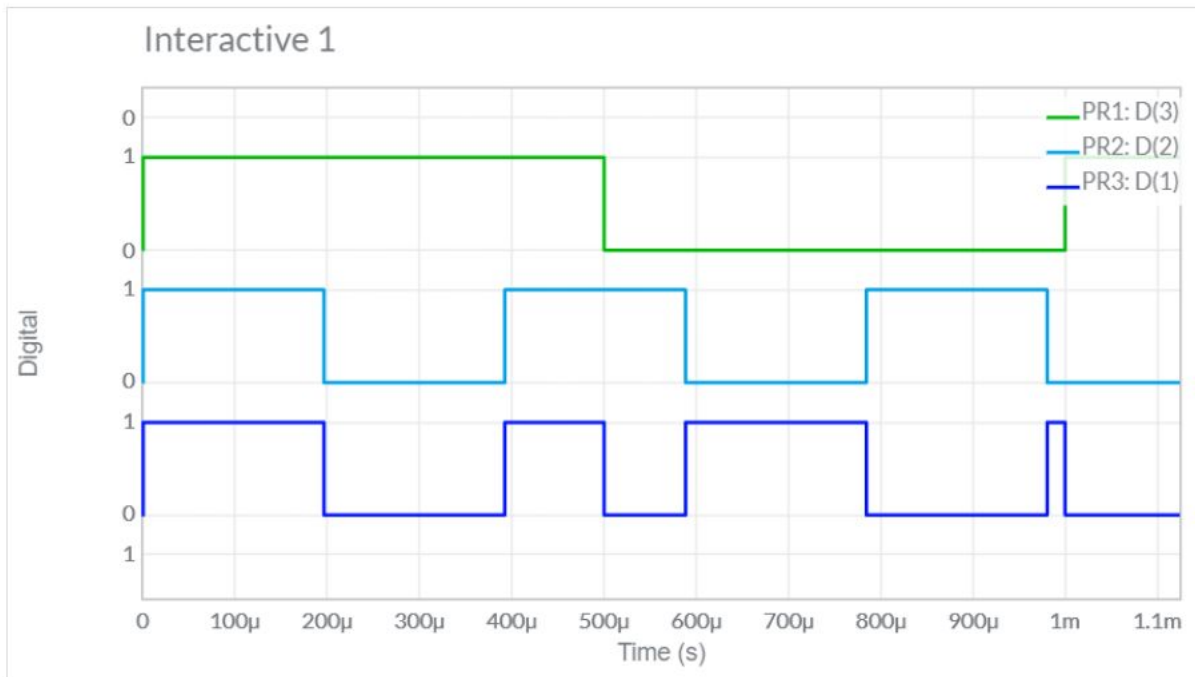

**NOT GATE**

## Circuit Graph

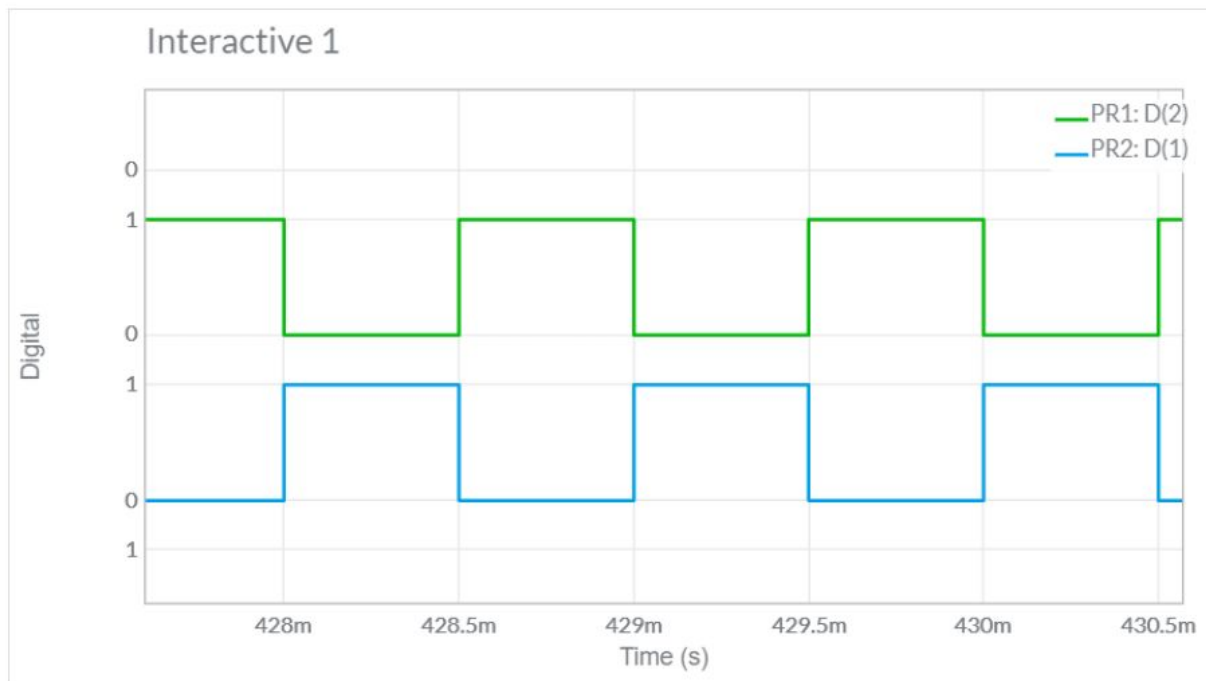

### PRECAUTIONS:

- Power supply should not exceed 5V.
- All the connections should be tight.
- Components should be tested before the practical.